



**BALOCHISTAN UNIVERSITY OF ENGINEERING AND TECHNOLOGY
KHUZDAR
DEPARTMENT OF BIOMEDICAL ENGINEERING**

B.E First Semester 2023


Assignment 01

Last Date: 30th October, 2023

| | | |
|--|---|--|
| <p style="text-align: center;">Question No. 1</p> | <p>Write Short note on the following terms</p> <ol style="list-style-type: none"> Kirchhoff's Current Law and Voltage Law Voltage Divider and Current Divider Rule Node, Loop, Mesh and Branch. Impedance and Admittance Inductive Reactance and Capacitive Reactance Impedance Triangle and Power Triangle. Source Transformation. Define Thevenin's Resistance and Thevenin Voltage J operator | |
| <p style="text-align: center;">Question No. 2</p> | <p>APPLY NODAL ANALYSIS TO FIND THE CURRENT I_3</p> | |

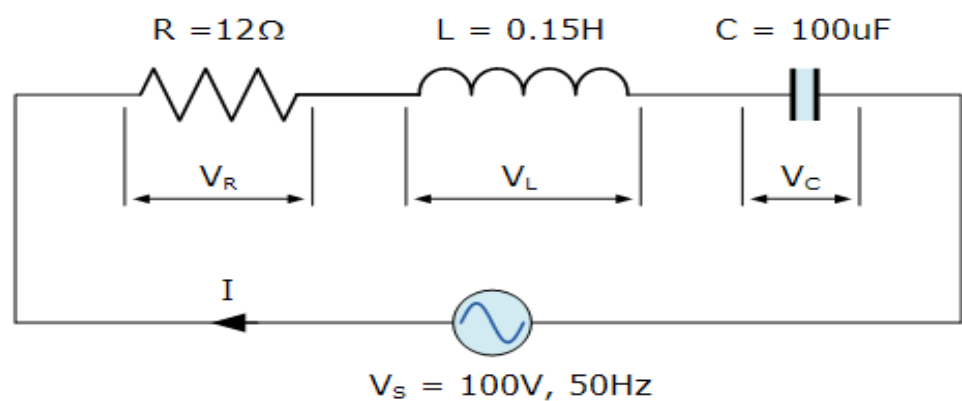
**Question
No. 3**


A series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of $100\mu\text{F}$ are connected in series across a 100V , 50Hz supply. Calculate the total circuit impedance, the circuits current, power factor and draw the voltage phasor



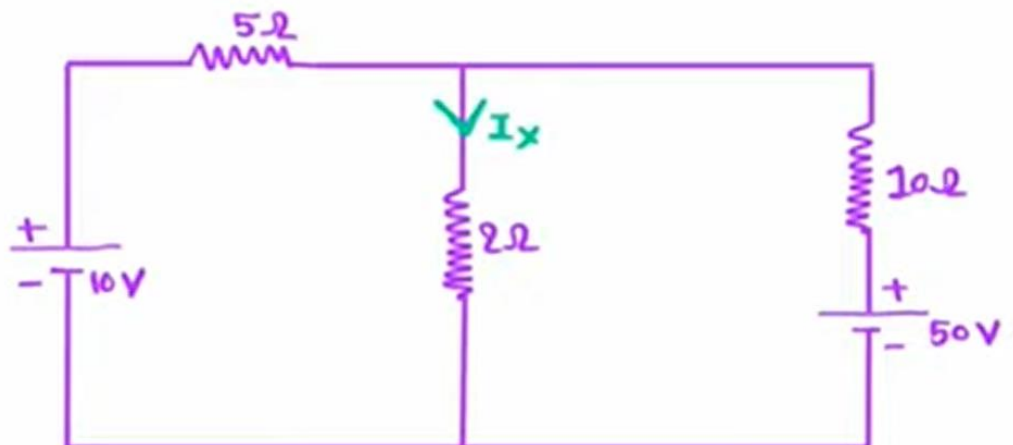**Question
No. 4**

Apply the Loop Analysis on the given below circuit, find the Current I_x


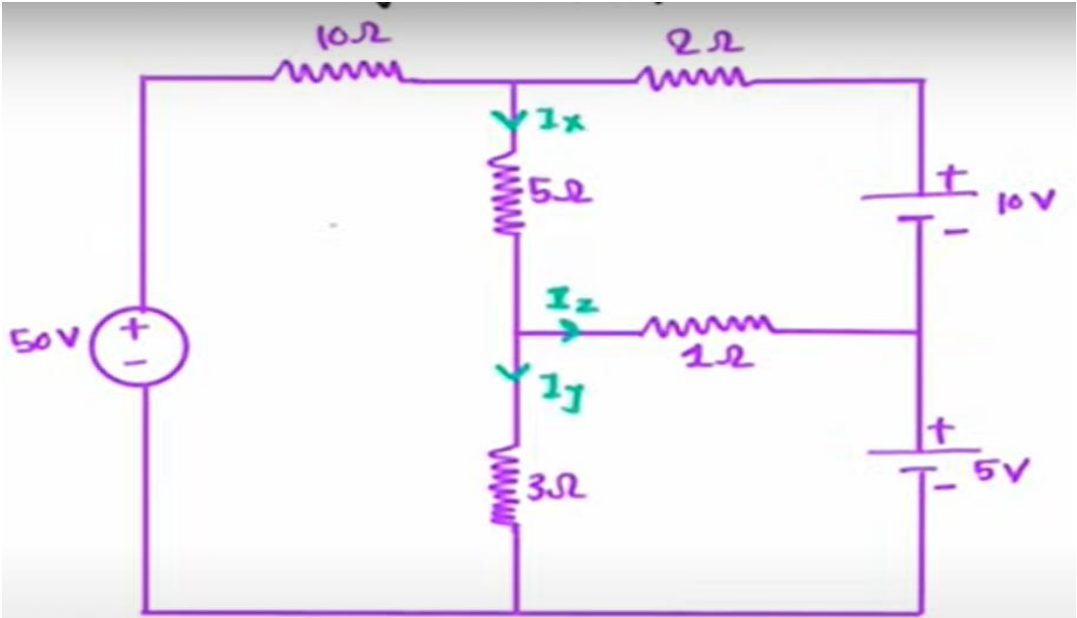
| | |
|----------------------------------|---|
| <p>Question No. 5</p> | <p>Apply the Loop Analysis on the given below circuit, find the Current I_x, I_y, and I_z</p>  |
| <p>Question No. 6</p> | <p>(a) Suppose $A = 4 + j1$ and $B = 2 + j3$ respectively. Determine the sum and difference of the two vectors in both rectangular ($a + jb$) form and graphically as an Argand Diagram.</p> <p>(b) Suppose $A = 4 + j1$ and $B = 2 + j3$ find the multiplication and division of A and B.</p> |
| <p>Question No. 7</p> | <p>(a) Convert Polar Form into Rectangular Form of $A = 6\angle 30^\circ$</p> <p>(b) Convert Rectangular Form into Polar Form $A = (5 + j3)$</p> |

*****BEST OF LUCK*****